

Figure 2. The loudness (mono) circuit


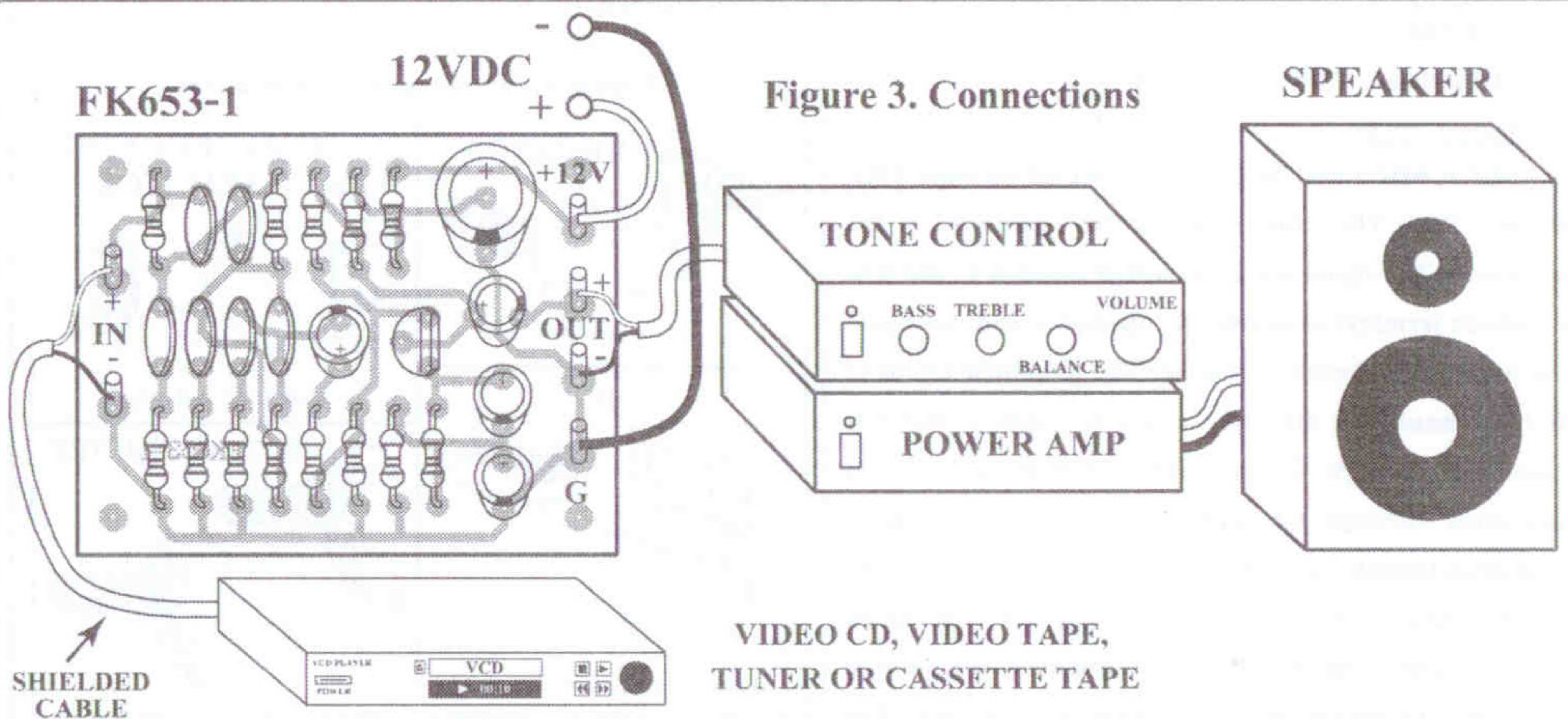


Figure 3. Connections

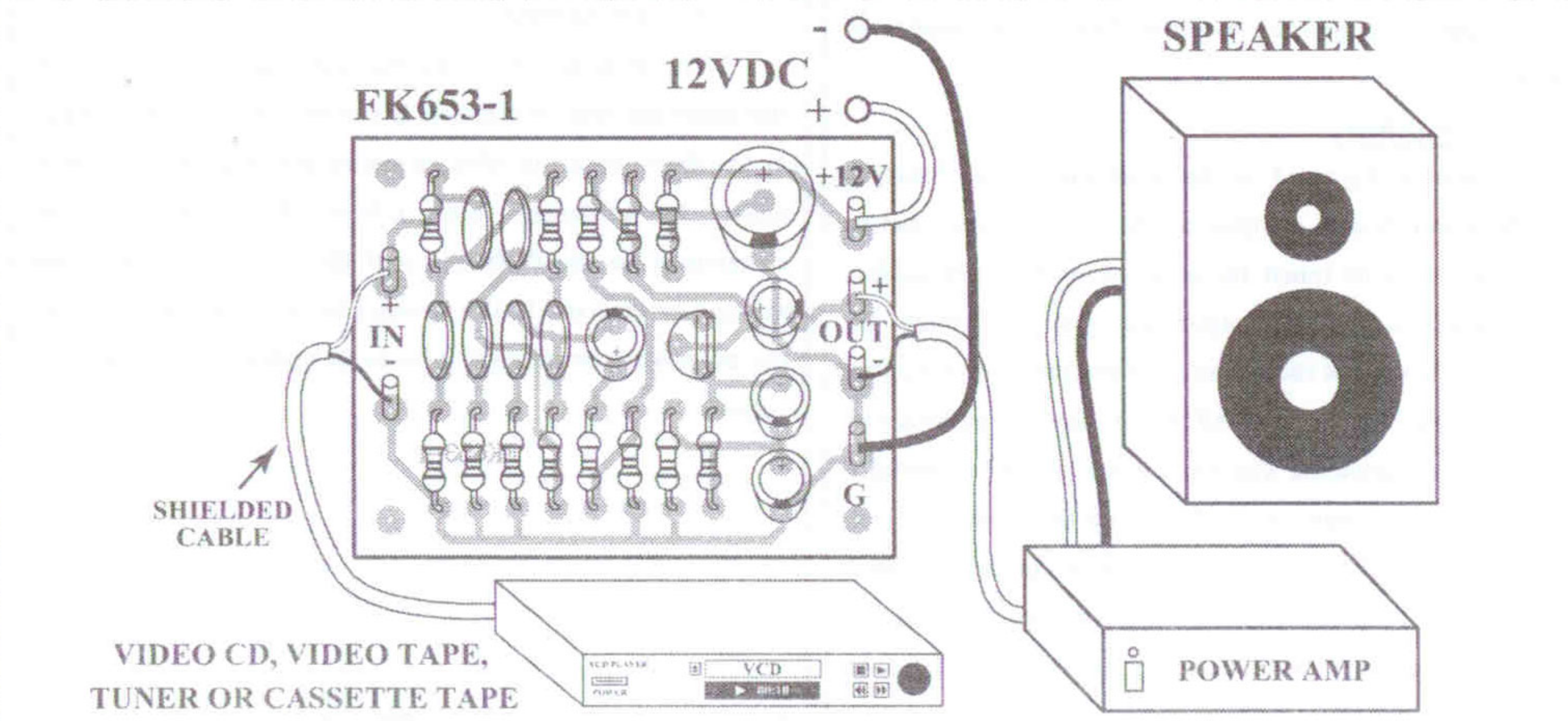

SPEAKER

VIDEO CD, VIDEO TAPE, TUNER OR CASSETTE TAPE

POWER AMP